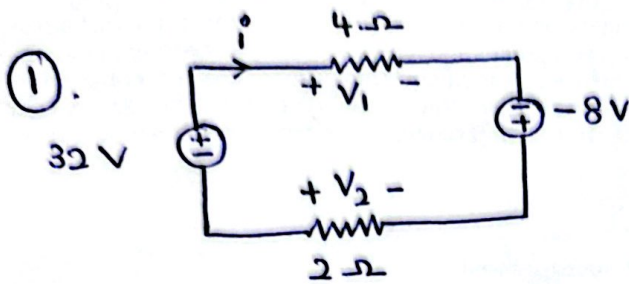


Assignment - 1



→ Use Kirchhoff's Voltage Law (KVL)
 $-32V + V_1 + (-8V) + V_2 = 0$

→ Use Ohm's Law,
 $V_1 = 4\Omega \cdot i$ $V_2 = 2\Omega \cdot i$

$$-32 + 4i - 8 + 2i = 0$$

$$-40 + 6i = 0$$

$$6i = 40$$

$$i = \frac{40}{6} = 6.67A$$

$$\rightarrow V_1 = 4 \times (6.67)$$


$$V_1 = 26.67V //$$

$$\rightarrow V_2 = 2i$$

$$V_2 = 2(6.67)$$

$$V_2 = 13.33V //$$

②.

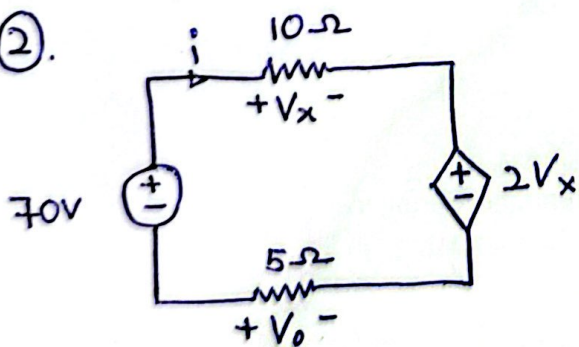

$2V_x \rightarrow$ KVL \rightarrow

$$-70V + 10i + 2V_x + 5i = 0$$

$$10i + 2(10i) + 5i = 70$$


$$35i = 70$$

$$i = \frac{70}{35} = 2A$$


$$V_0 = 5 \cdot i = 5(2) = 10V //$$

$$V_x = 10 \cdot i = 10(2) = 20V //$$

③.

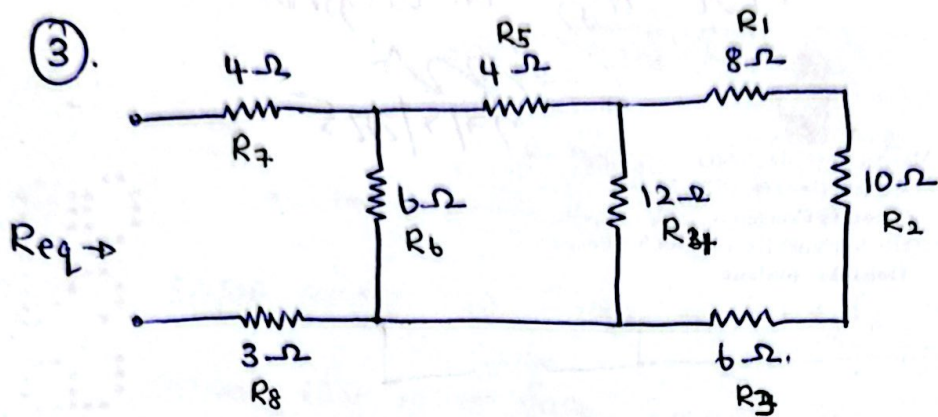

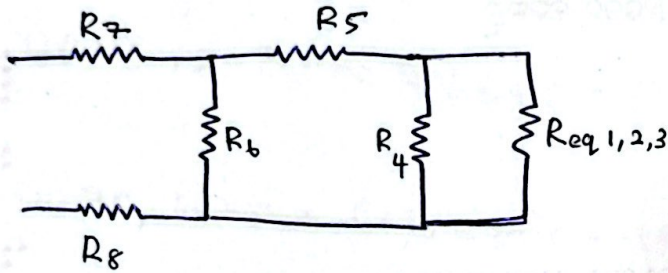
$$R_1, R_2, R_3 \rightarrow R_{eq1,2,3} = R_1 + R_2 + R_3 = 8 + 10 + 6 = 24 \Omega$$




$$R_{eq1,2,3}, R_4 \rightarrow R_{eq1,2,3,4} = \frac{(R_{eq})(R_4)}{(R_{eq}) + (R_4)} = \frac{(24)(12)}{(24) + (12)} = \frac{(24)(12)}{36} = 8 \Omega$$

$$R_{eq1,2,3,4} = 8 \Omega$$

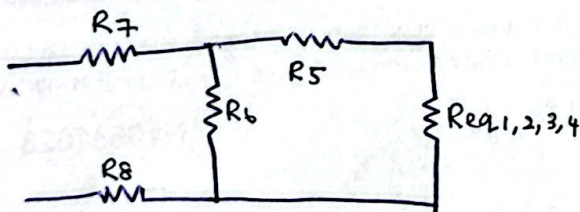

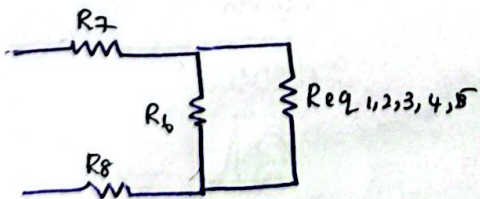
$$R_{eq1,2,3,4,5} = R_5 + R_{eq} = 4 + 8 = 12 \Omega$$



$$R_{eq1,2,3,4,5,6} = \frac{(R_6)(R_{eq})}{(R_6) + (R_{eq})} = \frac{6 \times 12}{6 + 12} = 4 \Omega$$

$$R_{eq1,2,3,4,5,6,7,8} = R_7 + R_8 + R_{eq1,2,3,4,5,6} = 4 + 3 + 4 = 11 \Omega$$
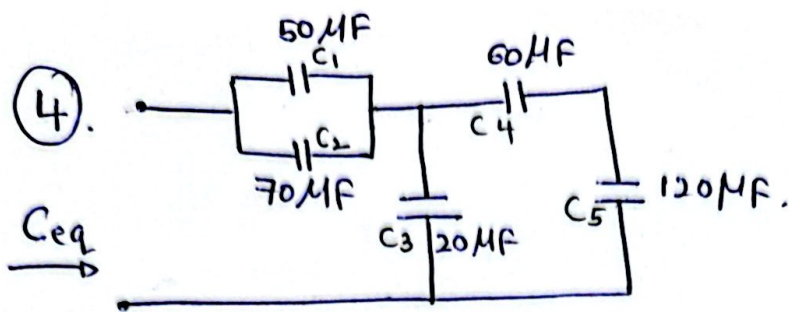
$$\therefore \underline{\underline{R_{eq} = 11 \Omega}}$$




$$50\mu F, 70\mu F \Rightarrow C_{eq1,2} = C_1 + C_2 = 50 + 70 = 120\mu F.$$

$$60\mu F, 120\mu F \Rightarrow C_{eq4,5} = \frac{(C_4)(C_5)}{C_4 + C_5} = \frac{(60)(120)}{180} = 40\mu F.$$

$$40\mu F, 20\mu F \Rightarrow C_{eq3,4,5} = C_3 + C_{eq4,5} = 20 + 40 = 60\mu F.$$

$$120\mu F, 60\mu F \Rightarrow C_{eq1,2,3,4,5} = \frac{(C_{eq1,2})(C_{eq3,4,5})}{(120) + (60)} = \frac{(120)(60)}{(180)} = 40$$
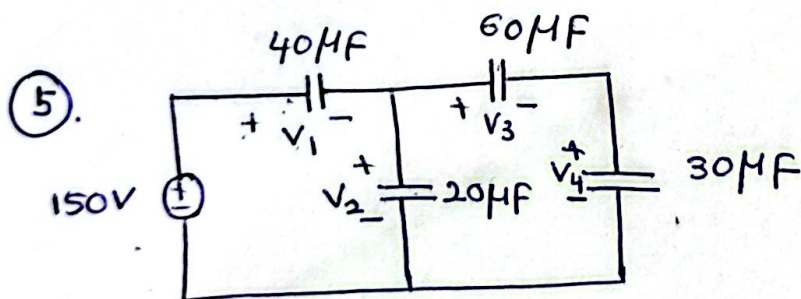
$$\therefore \underline{\underline{C_{eq} = 40\mu F}}$$



$$\rightarrow 60\mu F \text{ and } 30\mu F \text{ in series, } \rightarrow C_{eq} = \frac{(60)(30)}{90}$$

$$C_{eq} = 20\mu F.$$

$$\rightarrow 20\mu F \text{ and } 20\mu F \text{ in parallel, } \rightarrow C_{eq} = 20 + 20 = 40\mu F$$


~~40μF and 20μF in series, no.~~

Because of capacitance is equal (40μF and 40μF) the total voltage (150V) split exactly in half.

$$\therefore V_1 = 75V //$$

$$V_2 = 75V //$$

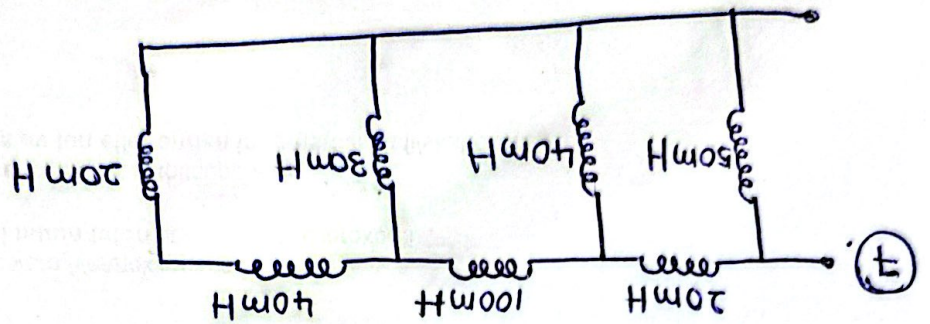
$$\begin{aligned}
 40\text{mH}, 20\text{mH} &\rightarrow L_{eq1} = 40 + 20 = 60\text{mH} \\
 60\text{mH}, 30\text{mH} &\rightarrow L_{eq2} = \frac{60 \times 30}{60 + 30} = 20\text{mH} \\
 20\text{mH}, 100\text{mH} &\rightarrow L_{eq3} = 20 + 100 = 120\text{mH}
 \end{aligned}$$



$$L_{eq1,2,3,4,5,6} = 6\text{H} + L_5 + L_6 = 9\text{H} + 4 + 8 = 18\text{H}$$

$$L_{eq1,2,3,4} = \frac{(42)(L_4)}{42 + (L_4)} = \frac{42(7)}{42 + 7} = 6\text{H}$$
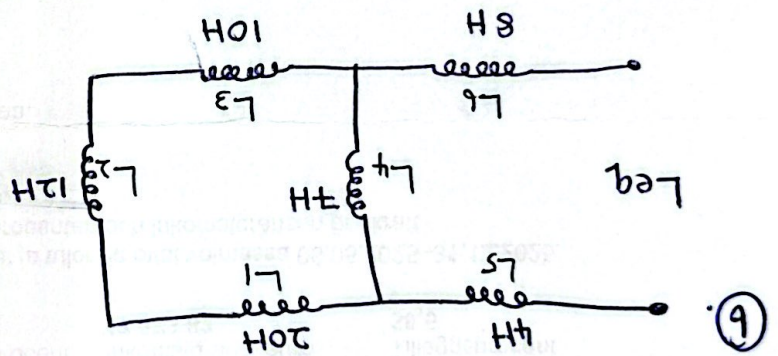
$$L_{eq1,2,3} = L_1 + L_2 + L_3 = 20 + 12 + 10 = 42\text{H}$$



$$\text{For } V_4 (30\text{mF}) \rightarrow V_4 = 75 \left(\frac{60 + 30}{90} \right) = 75 \left(\frac{90}{90} \right) = 50\text{V} //$$

$$\text{For } V_3 (30\text{mF}) \rightarrow V_3 = 75 \left(\frac{60 + 30}{90} \right) = 75 \left(\frac{90}{90} \right) = 25\text{V} //$$

$$V_x = V_{total} \cdot \left(\frac{C_{other}}{C_x + C_{other}} \right)$$

By Capacitance Voltage divider formula,

$$120\text{mH}, 40\text{mH} \rightarrow L_{eq4} = \frac{120 \times 40}{120 + 40} = \frac{120 \times 40}{160} = 30\text{mH}$$

$$30\text{mH}, 20\text{mH} \rightarrow L_{eq5} = 30 + 20 = 50\text{mH}$$

$$L_{eq} = \frac{50 \times 50}{50 + 50} = \frac{50 \times 50}{100} = 25\text{mH} //$$



33008209 046406 122802 2/1